

FACULTY OF ENGINEERING**B.E. 2/4 (CSE) I – Semester (Supplementary) Examination, July 2014****Subject : Logic and Switching Theory****Time : 3 hours****Max. Marks : 75****Note: Answer all questions from Part-A. Answer any FIVE questions from Part-B.****PART – A (25 Marks)**

- 1 Convert the given function into other canonical form. 3
 $F(x, y, z) = x + yz$
- 2 Write the Boolean expression and logic symbol for the given Truth table. 2

x	y	F
0	0	0
1	0	1
0	1	1
1	1	0

- 3 Realize the AND gate functionality using NOR-gates only. 3
- 4 Define the terms prime implicant and essential prime implicant. Give example. 2
- 5 Realize the function $F(x, y, z) = \Sigma (0, 1, 2)$ using multiplexers only. 3
- 6 Write a VHDL-code to design a 2-bit adder circuit. 3
- 7 Write the excitation and characteristic tables for JK and RS flip-flops. 2
- 8 Write the VHDL-code to design 2-bit counter. 2
- 9 Determine whether a given function $F(x, y, z) = x'y'z + xy'z' + x'yz'$ is symmetric or not. 3
- 10 Draw the relay contact network for the given function $F(a, b, c) = a + b'c$. 2

PART – B (50 Marks)

- 11 a) Represent the given decimal number into octal, hexadecimal and binary form. 6
 i) $(12.50)_{10}$ ii) $(34.25)_{10}$
- b) Convert the given function into canonical sum-of-products and canonical product-of-sums form. 4
 $F(A, B, C) = AB' + C'$
- 12 a) Simplify the Boolean function into minimum number of literals using K-map method. 5
 $F(w, x, y, z) = \Sigma (0, 3, 5, 9, 11) + \Sigma_d (1, 2)$
- b) Simplify the function using tabulation method. 5
 $F(x, y, z) = \Sigma (0, 1, 2, 3, 6, 7)$