Code No. 6059 / M

## FACULTY OF ENGINEERING B.E. 2/4 (ECE) II – Semester (Main) Examination, June 2014

## Subject: Networks and Transmission Lines

## Time: 3 Hours

Max.Marks: 75

Note: Answer all questions from Part A. Answer any five questions from Part B. PART – A

- 1 Find the characteristic impedance of the network shown below: (3)1000 2 10002 800 M Define image transfer constant and iterating transfer constant of a Network. 2 (2) Find the cutoff frequency of the filter shown (2) 3 IOmH 10 mH 1002  $\sim$ T 50MF What are advantages of 'm' - derived filter over constant K filter? 4 (2)Derive the relation between nepers and decibels. 5 (3)Test whether the polynomial  $P(S) = S^3 + 4S^2 + 5S + 2$  is Hurwitz. 6 (3)Mention any two important functions of an equalizer. 7 (2) 8 Show that 1/4 transformer acts like a impedance inverter. (3) Find the attenuation in dB due to the following network. 9 (3) 100 m 100 A 50 N
- 10 What are the applications of Smith chart?

(3)

0

## PART – B

11 (a) Find the image impedances of the following network.



- (b) Derive the expression for characteristic impedance of a symmetrical lattice network. (5)
- 12 (a) Design a composite High pass filter with a cut-off frequency of 15 KHz and a nominal impedance of 600  $\Omega$  with frequency of infinite attenuation is 14 KHz. (6) (4)
  - (b) Justify that m=0.6 for m-derived terminating half section.
- 13 (a) the driving point impedance of a LC Network is given by  $Z(S) = S^4 + 4S^2 + 3/S^3 + 2S$ . Determine the second caver form of the network.
  - (b) Design a symmetrical T attenuator with an attenuation of 60 dB and a nominal impedance of  $600 \Omega$ .
- 14 (a) A 12 Km line is terminated by its characteristic impedance. At a certain frequency the voltage at 1 Km from the sending end is 10% below that of input. Calculate VSWR.
  - (b) A transmission line 50 Km long gave the following results of impedances at 700 Hz,  $Z_{OC} = 328 \frac{|-29.2^{\circ}|}{|-29.2^{\circ}|}$  and  $Z_{SC} = 1543 \frac{|6.3^{\circ}|}{|6.3^{\circ}|}$  determining the line constants.
- 15 (a) Define reflection coefficient, VSWR. Derive the equation for input impedance of a loss-less transmission line.
  - (b) Explain briefly stub matching.
- 16 (a) A certain line has a characteristic impedance  $600\Omega$  determining the standing wave ratio when  $Z_R = 650 - j 475$  ohms.
  - (b) What are applications of Smith chart? Explain.
- 17 (a) The VSWR measured on UHF transmission line working at a frequency of 300 MHz is found to be 'z' if the distance between load and voltage minimum is 8 metre. Calculate the value of load impedance.
  - (b) Explain with neat circuit diagram, how to measure the primary constants of a transmission line experimentally.

(5)