

FACULTY OF ENGINEERING

B.E. 2/4 (EE/Inst.) I – Semester (Supplementary) Examination, July 2014

Subject : Electronic Engineering - I

Time : 3 hours

Max. Marks : 75

Note: Answer all questions from Part-A. Answer any FIVE questions from Part-B.**PART – A (25 Marks)**

- | | | |
|----|---|---|
| 1 | Distinguish between zener breakdown and avalanche breakdown. | 3 |
| 2 | What is the role of bleeder resistance in a rectifier circuit using an LC filter? | 2 |
| 3 | Explain the concept of base width modulation. | 2 |
| 4 | What do you understand by transistor biasing? Why is it necessary to bias a transistor? | 3 |
| 5 | Explain why E-MOSFET is called normally off MOSFET. | 3 |
| 6 | Draw the small signal equivalent model of FET. | 3 |
| 7 | Why do we need more than one stage of amplifiers in practical circuits? | 2 |
| 8 | State Miller's theorem. | 2 |
| 9 | Explain about the effect of emitter by pass capacitor on LF response. | 3 |
| 10 | Why coupling capacitors are not required in a transformer coupled amplifier? | 2 |

PART – B (50 Marks)

- | | | |
|----|--|----|
| 11 | a) What is a rectifier? Derive the expression for ripple factor of a full-wave center-tapped rectifier. | 6 |
| | b) Explain the V-I characteristics of a p-n junction diode using the current equation. | 4 |
| 12 | a) Explain how h-parameters can be calculated from static characteristics. | 6 |
| | b) Compare CB, CE and CC configuration. | 4 |
| 13 | a) Explain the construction, operation and characteristics of a JFET with necessary Diagrams. | 7 |
| | b) What is the difference between the enhancement and depletion MOSFETs. | 3 |
| 14 | a) Explain the construction, operation and characteristics of UJT. | 7 |
| | b) List out the differences between DIAC and TRIAC. | 3 |
| 15 | a) Explain in detail about difference amplifier. | 5 |
| | b) Discuss in detail various types of distortions in amplifiers. | 5 |
| 16 | Discuss the effect of cascading multiple stages of amplifier sections over gain and bandwidth of the overall amplifier. Derive the expressions for overall gain for n-stage cascaded system. | 10 |
| 17 | Write short notes on : | |
| | a) Transistor as an amplifier | 5 |
| | b) Transformer coupled amplifier | 5 |
