

FACULTY OF ENGINEERING
B.E. 2/4 (EEE) II - Semester Examination, June 2014

Subject : Electrical Circuits - II

Time : 3 Hours


Max. Marks: 75

Note: Answer all questions of Part - A and answer any five questions from Part-B.
PART – A (25 Marks)


- 1 Explain the initial conditions in R, L and C in respect of Transient analysis. (3)
- 2 A 5 μF condenser is connected through a 1000 K Ω resistor to a DC source 10V. After being charged for half minute, the condenser is disconnected and discharged through a resistor R. Determine the energy dissipated in R. (3)
- 3 State Initial and final value theorems in Laplace transform. (3)
- 4 Obtain the current response of RC parallel circuit for unit step input using Laplace transformation. (3)
- 5 Define Transfer function and its Limitations. (3)
- 6 Find the current response $i(t)$ if $I(s) = \frac{2s^2 + 3s + 2}{s^2 + 2s - 3}$. (4)
- 7 Check whether the following polynomial is Hurwitz or not? (3)
 $P(s) = 2s^6 + s^5 + 13s^4 + 6s^3 + 56s^2 + 25s + 25$
- 8 Define half-wave symmetry in Fourier series. (3)

PART – B (50 Marks)

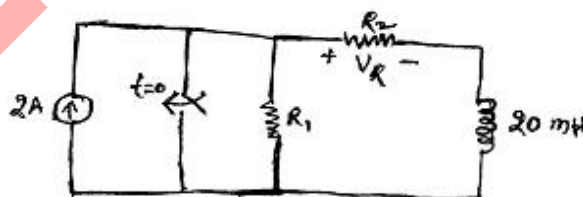- 9 The switch is open for a long time and is closed at $t = 0$. Find the values of R_1 and R_2 in the circuit given in figure 1. if $V_R(0^+) = 10\text{V}$ and $V_R(1, \text{msec}) = 5\text{V}$. (10)




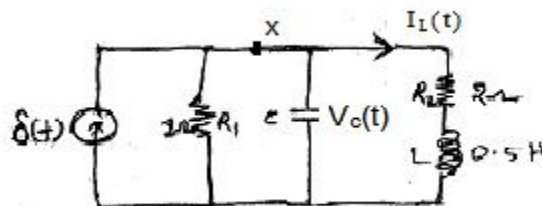- 10 Find $V_c(t)$ and $I_L(t)$ in the circuit of figure 2 assuming zero initial conditions. (Use Laplace transformation). (10)




- 2 -

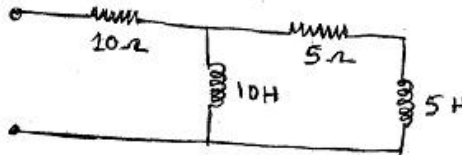- 11 Obtain the pole zero plot in the s-plane of the driving point impedance function for the network shown in figure 3. (10)



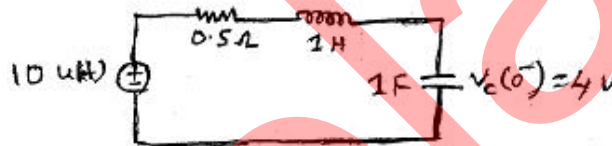- 12 Find $i(t)$ using Laplace transform for the circuit shown in figure 4 if the initial voltage on the capacitor is 4v. Assume zero initial condition for the inductor. (10)



- 13 (a) Write all the properties of positive Real functions. (4)
 (b) Check whether the given $p(s)$ is positive Real or not?
 $p(s) = s^5 + 7s^4 + 5s^3 + s^2 + 2s + 4$. (6)
- 14 (a) Find the Fourier transforms for the following functions (5)
 (i) $\sin(4t+30)$ (ii) $u(t+2)$
 (b) State and explain complex Translational theorem. (5)

- 15 Realize $Z(s) = \frac{s(s^2 + 2)(s^2 + 4)}{(s^2 + 1)(s^2 + 3)(s^2 + 5)}$ in both Foster and forms. (10)
