

**FACULTY OF INFORMATICS****B.E. 2/4 (IT) I – Semester (Supplementary) Examination, July 2014****Subject : Micro Electronics****Time : 3 hours****Max. Marks : 75****Note: Answer all questions from Part-A. Answer any FIVE questions from Part-B.****PART – A (25 Marks)**

- |    |   |   |
|----|---|---|
| 1  | Differentiate between intrinsic and extrinsic semiconductor.                                  | 2 |
| 2  | What is a varactor diode? Show its circuit symbol and explain its operation.                  | 3 |
| 3  | Differentiate between JFET and MOSFET.  | 3 |
| 4  | What are the advantages of negative feedback in an amplifier?                                 | 2 |
| 5  | Give the Barkhausen conditions required in order for sinusoidal oscillations to be sustained. | 2 |
| 6  | Define the conversion efficiency $\eta$ (eta) of a power amplifier.                           | 2 |
| 7  | Draw the output circuit of a class B power amplifier.   | 3 |
| 8  | Define the following with respect to operational amplifier                                    | 2 |
|    | i) CMRR                      ii) Slew rate  |   |
| 9  | Draw a circuit of zero crossing computation and show the O/P for the given sinusoidal input.  | 3 |
| 10 | List the different terminals of MOSFET.   | 2 |

**PART – B (50 Marks)**

- |    |  |         |
|----|--|---------|
| 11 | a) What is a limiter? Explain the operation of any two clipper circuits.   | 6       |
|    | b) How does the varactor diode function as a variable capacitor. Explain?  | 4       |
| 12 | a) Draw the h-parameter small signal model of BJT at low frequency using all four parameters.  | 4       |
|    | b) Draw and explain the biasing circuits for a JFET.   | 6       |
| 13 | a) What are the causes of cross over distortion? What are the methods to overcome it. Explain?   | 4       |
|    | b) Draw and explain the operation of any one LC oscillator.  | 6       |
| 14 | a) Define a    i) Class A        ii) Class B and        iii) Class AB amplifier.   | 4       |
|    | b) Explain the characteristics of power MOSFET.  | 6       |
| 15 | Design and explain the operation of a triangular wave generator using operational amplifier.   | 10      |
| 16 | Explain the operation of BJT as different amplifier circuits. Compare the characteristics of above circuits with respect to input impedance, $A_V$ , $A_I$ , and output conductance. | 10      |
| 17 | Write short notes on the following :   |         |
|    | a) Ideal OP-Amp integrator                      b) Distortions in power amplifier  | (5 + 5) |

\*\*\*\*\*