

FACULTY OF ENGINEERING
B.E. 3/4 (EE/Inst.) I-Semester (Suppl.) Examination, July 2014

Subject : Power Electronics

Time : 3 Hours

Max. Marks: 75

Note: Answer all questions of Part - A and answer any five questions from Part-B.

PART – A (25 Marks)

- 1 What are the different types of power diodes? State the limitations of Schottky diodes. (3)
- 2 Compare IGBT and MOSFET. (2)
- 3 Explain the steady state characteristics of a GTO. (3)
- 4 What is the difference between Forced commutation and Line commutation? Explain. (2)
- 5 Explain the effect of introducing freewheeling diodes in phase controlled converters. (2)
- 6 Derive the expression for average output voltage of a single phase half controlled converter for R load. (3)
- 7 Explain any one scheme of Time ratio control of choppers. (3)
- 8 List the advantages and disadvantages of single phase half wave AC regulator. (2)
- 9 Discuss the advantages and disadvantages of a Voltage source inverter compared to a current source inverter. (3)
- 10 What are the advantages of sinusoidal pulse width modulation? (2)

PART – B (50 Marks)

- 11 (a) Explain the switching characteristics of power MOSFET. (5)
 (b) Explain the dynamic characteristics of a power BJT. (5)
- 12 (a) Explain the over voltage and over current protection of thyristor. (5)
 (b) Explain the turn off mechanism in a power MOSFET. (5)
- 13 Explain the working of a three phase half controlled rectifier with RLE load. Also draw the relevant waveforms. (10)
- 14 The step down chopper has a resistive load of $R = 10 \text{ ohm}$ and the input voltage is $V_{DC} = 200\text{V}$. When the chopper is turned on, the voltage drop across the switch is 1 V , the chopper frequency if $f = 1 \text{ kHz}$. If the duty cycle is 40% , determine (10)
 - (a) the average output voltage
 - (b) the RMS output voltage
 - (c) Efficiency of the chopper
- 15 (a) Explain the working of a single phase AC voltage controller with RL as load. (7)
 (b) Write the applications of choppers and cyclo converters. (3)
- 16 Explain the principle of sinusoidal pulse width modulation scheme with relevant waveforms and necessary equations. (10)
- 17 Write short notes on the following: (10)
 - (a) Multilevel inverters
 - (b) Class-E chopper
