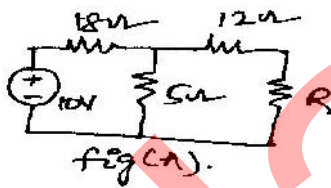


FACULTY OF ENGINEERING**B.E. 2/4 (ECE) I – Semester (Main) Examination, November 2013****Subject : Basic Circuits Analysis****Time : 3 hours****Max. Marks : 75****Note: Answer all questions from Part–A. Answer any FIVE questions from Part–B.****PART – A (25 Marks)**


1. State and explain superposition theorem. 3
2. What are the properties of incidence matrix? 2
3. Find the value of 'R' in fig shown in (A) in such a way that maximum power is transferred to it. 3



4. Write the difference between transient and steady state responses. 3
5. State and explain the time constant of an R-L circuits. 2
6. Define apparent and average powers. 2
7. Define and explain ABCD parameters of a network. 3
8. What is the condition of reciprocity for hybrid parameters and also the condition of symmetry? 2
9. Define : Incidence matrix and Tie set. 2
10. Define : Complex frequency, poles and zeros of a transfer function. 3

PART – B (50 Marks)

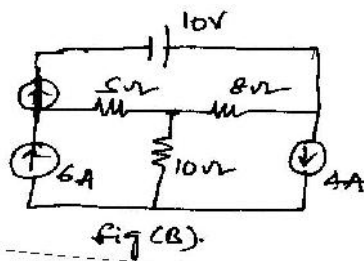- 11.a) For the circuit shown in fig (B), find the node voltages using nodal analysis. 8




- b) Define and classify energy sources. 2

..2

- 2 -

- 12.a) Determine the impedance connected across the terminal A & B in fig (C), for the maximum power transfer. Also find value of max. power transferred.

8

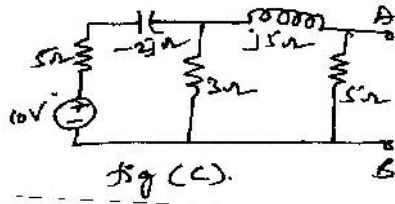


- b) Define self and mutual inductances.

2

13. Find the response $v(t)$ in the circuit of fig.(D). Also plot it with neat sketches.

10

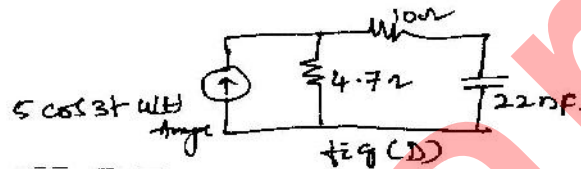

- 14.a) Show that, "when networks are interconnected in series-parallel manner, then the overall h-parameters are the summation of individual h-parameters of networks interconnected".


8

- b) Define reciprocity theorem and explain.

2

15. For the network shown in fig(E), write a cut-set schedule. Obtain the values of branch voltages and branch currents.

10

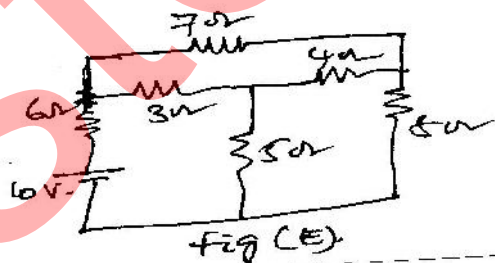

- 16.a) What the restrictions on the location of pole-zeros of a transfer function, explain?

5

- b) The Laplace transform of current $I(s)$ in a network is given by

$$I(s) = \frac{3s}{(s+2)(s+3)}$$

Plot poles and zeros in the s-plane and hence obtain the time-domain response.

5

17. Write short notes on :

10

- Series and parallel resonances
- Principle of Duality
- Zero input response and zero state responses.
