
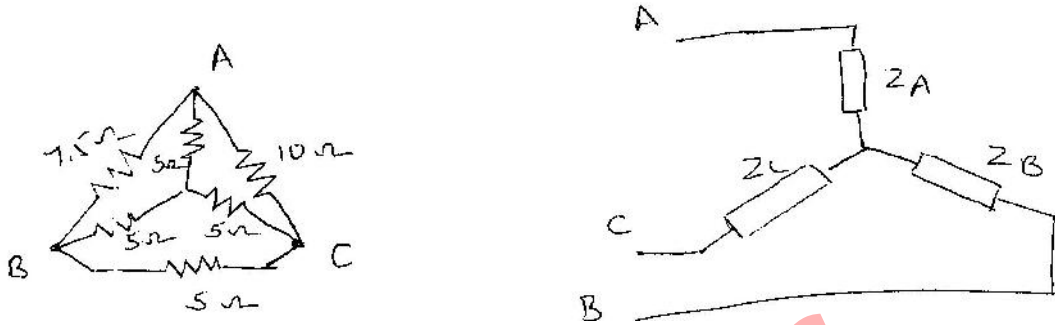


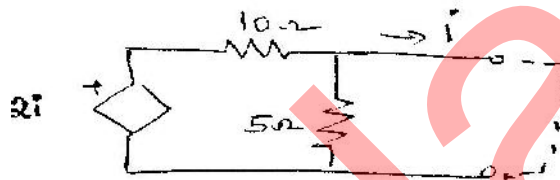9. Obtain the value of star connected equivalent impedance Z_A of the circuit given. 3




10. The Thevenin's resistance of the circuit shown is 3



PART - B (50 Marks)


11.a) Explain in detail different classifications of circuit elements. 4

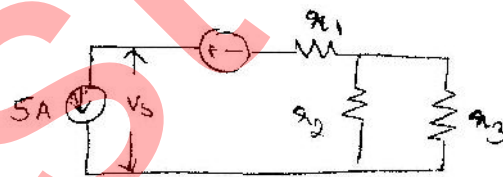b) Find V_S if $r_1 = 2\Omega$, $r_2 = 1\Omega$ and $r_3 = 5\Omega$ 6




12.a) Explain the concept of Duality in electrical networks. 4

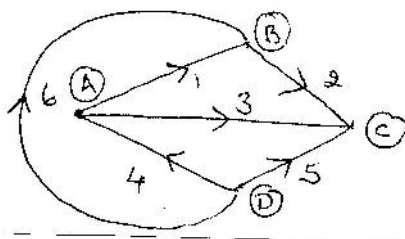b) Write the basic cutset matrix and tieset schedule for the graph of a network shown selecting 1, 2, 4 as tree. 6



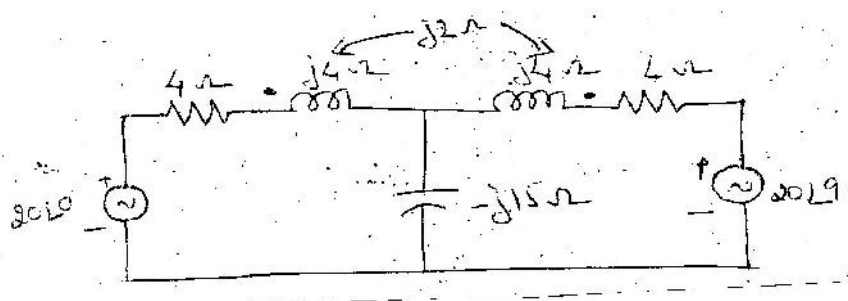13. Determine the voltage across the capacitor in the circuit shown below 10



FACULTY OF ENGINEERING

B.E. 2/4 (EEE) I – Semester (Main) Examination, November 2013

Subject : Electrical Circuits – I


Time : 3 hours

Max. Marks : 75


Note: Answer all questions from Part-A. Answer any FIVE questions from Part-B.

PART – A (25 Marks)

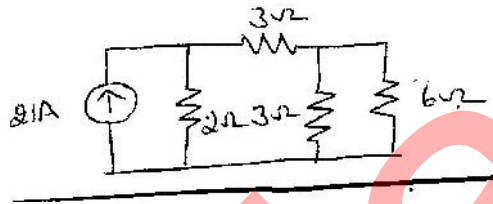1. Determine the current through 6Ω resistor and power supplied by the current source. 3




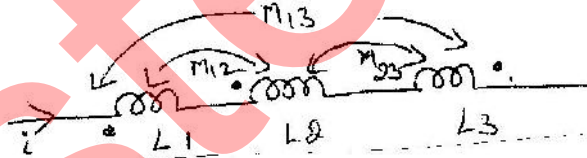2. Two watt meters are used to measure the power in a 3 phase balanced circuit. What is the power factor of the load when both meters read equal? 2
3. Differentiate between dependent and independent sources. 2
4. Find the total inductance of three series connected coupled coils. 3




Given $L_1 = 1H$ $L_2 = 2H$ $L_3 = 5H$ $M_{12} = 0.5H$ $M_{23} = 1H$ $M_{13} = 1H$

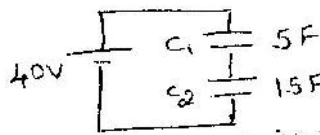5. The voltage across $5F$ capacitor in the circuit is 2




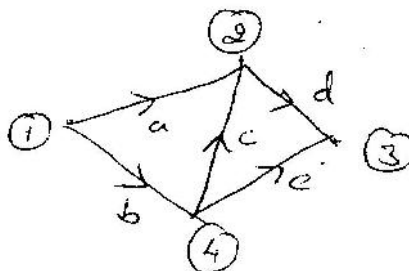6. Write the incidence matrix of the oriented graph given below. 3




7. Given $y_{11} = 10 \bar{U}$, $y_{22} = 5 \bar{U}$, $y_{12} = y_{21} = 2 \bar{U}$ find z_{21} . 2
8. In a series resonant circuit, the capacitance has been doubled. Then the new resonant frequency will become _____ times the original resonant frequency. 2

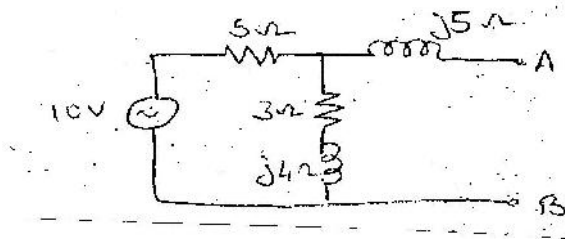- 14.a) Obtain the Thevenin's equivalent circuit for the active network shown in figure. 5




- b) Compute the form factor and peak factor of a half wave rectified sinusoidal wave form. 5

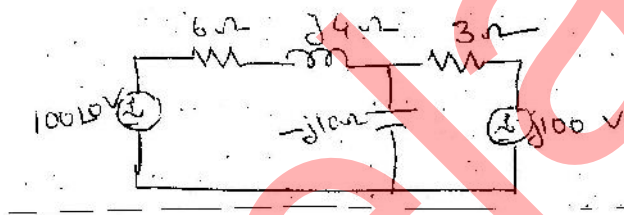
15. Both sources shown in figure are operating at the same frequency. Find complex power generated by each source and the complex power absorbed by each passive circuit element. 10



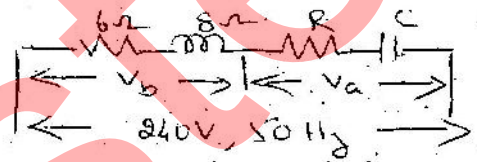- 16.a) Find the values of R and C in the circuit shown so that $V_b = 4V_a$ 5



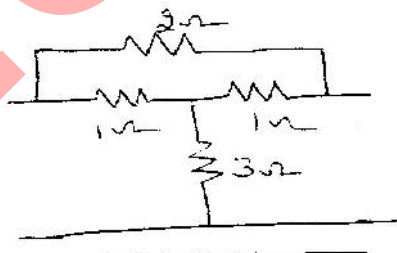- b) Obtain the open circuit parameters of the circuit shown in figure. 5



- 17.a) Draw the phasor diagram of a balanced Δ connected system showing the relation between phase and line quantities of currents and voltages. 5

- b) Find the neutral shift voltage of the network shown. The supply voltages are balanced with magnitude $E_a = 230 \angle 0^\circ$, $E_b = 230 \angle -120^\circ$ and $E_c = 230 \angle +120^\circ$ 5

