

FACULTY OF ENGINEERING

B.E. 2/4 (Civil) II Semester (Main) Examination, May/June 2011

ELECTRICAL TECHNOLOGY (PART – A)

Time : 1½ Hours]

[Max. Marks : 38

Note : Answer all questions from Part – A. Answer any three questions from Part – B.

PART – A

(Marks : 14)

1. Derive the power loss in resistive element. 2
2. Through a resistor of value 2 Ohms a current of $i(t) = 2 \sin 50t$ is passed. What is the voltage across its terminals ? 3
3. Define rms value of a.c. quantity. 2
4. Draw the phasor diagram of transformer on load at unity power factor. 2
5. Derive the torque equation of 3- ϕ induction motor. Draw the speed-torque characteristics. 3
6. Define the term "illumination". 2

PART – B

(Marks : 24)

7. Derive the expression for power in 3- ϕ circuit. 8
8. A 1-phase, 250/500 V, transformer gave the following results : 8
 O.C. test : 250 V, 1 A, 80 W on L.V. side
 S.C. test : 20 V, 12 A, 100 W on L.V. side
 Calculate the parameters of equivalent circuit.
9. Explain with neat-sketches the principle of operation of a 3-phase induction motor. 8
10. (a) Derive the emf equation of a 1- ϕ transformer. 3
 (b) Derive the expression for voltage regulation of a 1- ϕ transformer. 5
11. (a) Explain with an example on street lighting calculations. 5
 (b) A 4-pole, 50 Hz induction motor runs with 4% slip at full-load. What will be the frequency of current induced in the rotor (i) at starting (ii) at full load ? 3