

FACULTY OF ENGINEERING
B.E. 2/4 (E & EE) I Semester (Main) Examination, December 2010
ELECTRICAL CIRCUITS – I

Time : 3 Hours]

[Max. Marks : 75


Note : Answer all questions from Part – A. Answer five questions from Part – B.

(2.5×10=25 Marks)

1. Find the power absorbed by an element for $t = 10$ sec if the current is


$$2e^{-0.1t} \text{ and voltage across the element is } V = \frac{6 di}{dt} \quad 2$$

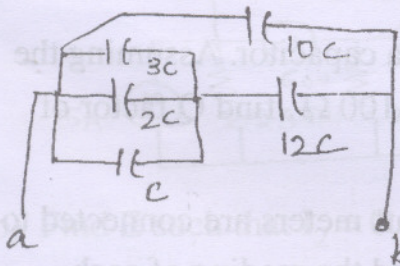2. Find the equivalent capacitance for the given combination. 3



3. State and explain Reciprocity theorem and give its application. 3

4. In the network shown find X_L . 2

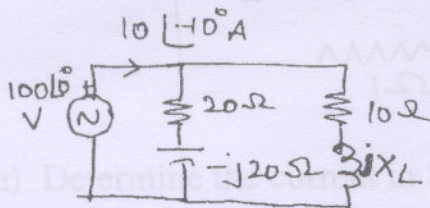


5. The current in a circuit lags the voltage by 30° . If the input power be 480 W and supply voltage be $V = 100 \sin(377t + 20^\circ)$. Find the complex power. 2



6. What is the rms value of the periodic waveform shown, where Time period $T = 4$ sec ?

3

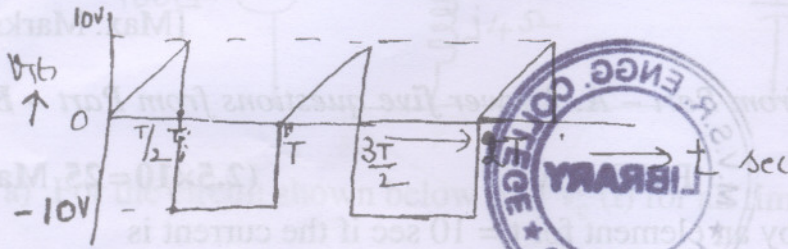

7. A dc voltage of 20V is applied to an RL circuit where $R = 5 \Omega$ and $L = 10H$.

Find

- The time constant and
 - Maximum value of energy stored.
8. A coil produces resonance at 20 KHz in series with a capacitor. Assuming the inductance and resistance of the coil to be 10H and 100Ω , find Q factor of the coil.
9. A 3ϕ 400V load has a power factor of 0.4. Two Watt meters are connected to measure the power. If the input power be 10KW. Find the reading of each instrument.
10. How filters are classified? mention the different types of filters.

2

2

3


3

PART - B

(5×10 = 50 Marks)

11. a) Find the power loss in 1Ω resistor.


4

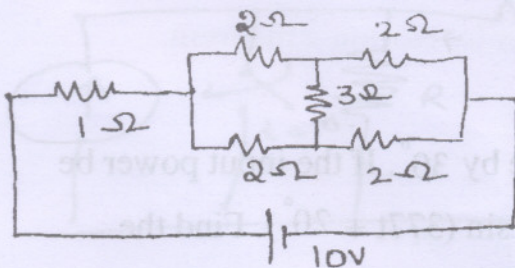




b) A current wave $i(t)$ is applied to an inductance of $10H$. Find $V(t)$ and sketch it.

6

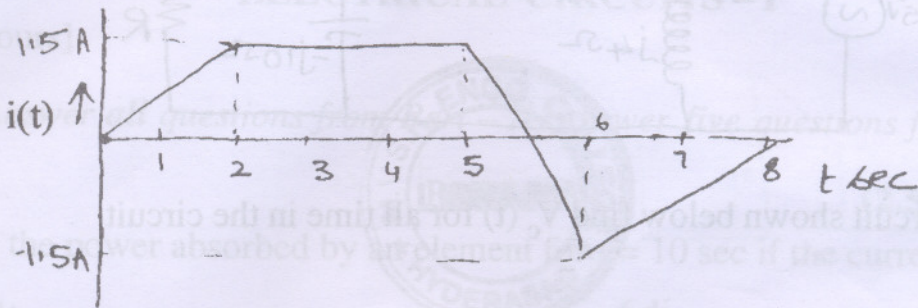


12. a) Find the voltage across 40Ω resistor and the power supplied by $5A$ source using Nodal analysis method.

6

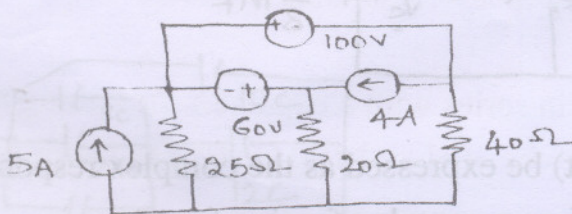


b) Find E such that $I_2 = 0$.

4

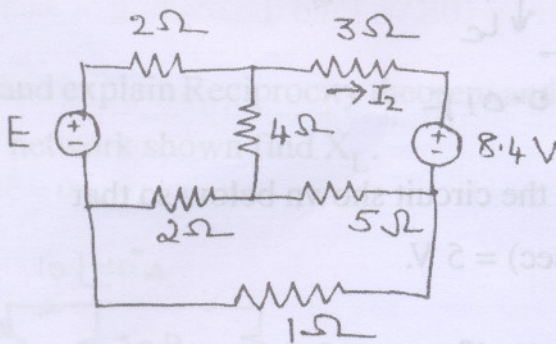


13. a) Determine the current in 8Ω resistor by Norton's theorem.

5

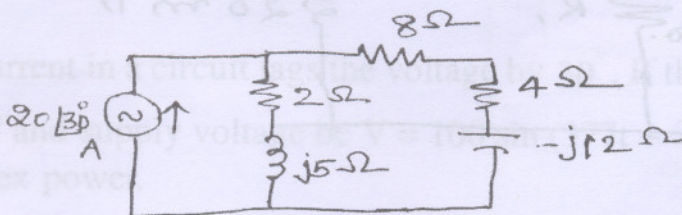




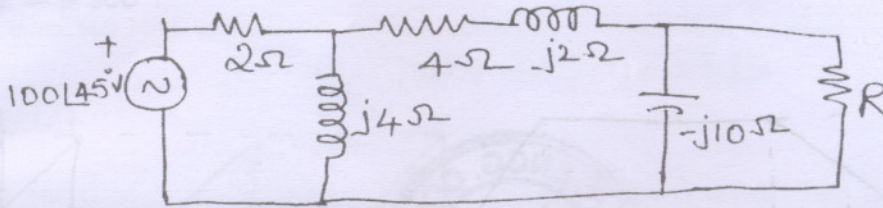
- b) Determine the value of R so that maximum power is transferred to it. 5



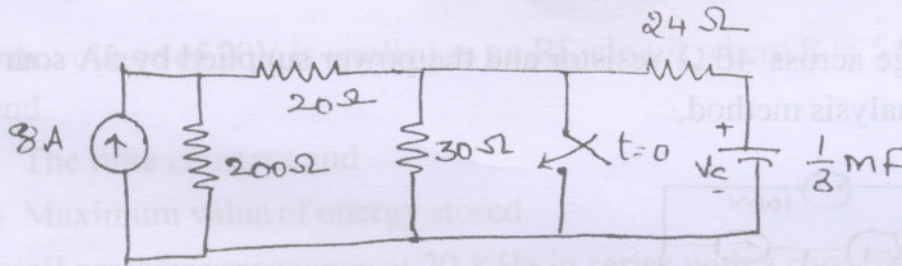
14. a) For the circuit shown below find $V_c(t)$ for all time in the circuit. 5



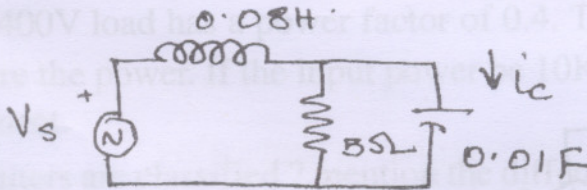- b) In the circuit shown below let $i_c(t)$ be expressed as the complex response $20e^{j(40t + 30^\circ)}$ A and express V_s as a complex forcing function. 5



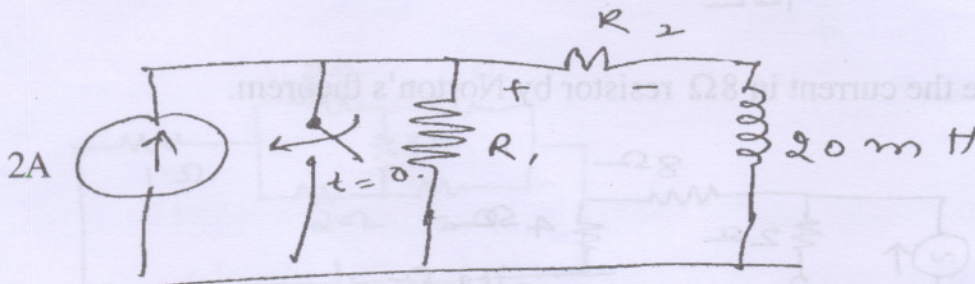
15. a) Select the values of R_1 and R_2 in the circuit shown below so that $V_{R_2}(0^+) = 10$ V and $V_{R_2}(1 \text{ m sec}) = 5$ V. 5



b) A series combination of $12\ \Omega$ resistance and $600\ \mu\text{F}$ capacitance is connected to a $220\ \text{V}$, $50\ \text{Hz}$ supply. Estimate the current, active power, reactive power and apparent power. Draw the phasor diagram. 5

16. a) A RLC series circuit is to be designed to produce a magnification of 5 at $1000\ \text{rad/sec}$. A $120\ \text{V}$ source is connected to RLC series circuit can supply maximum current of $8\ \text{A}$. The half power frequency impedance of the circuit is $32\ \Omega$. Find the values of R , L and C . 5

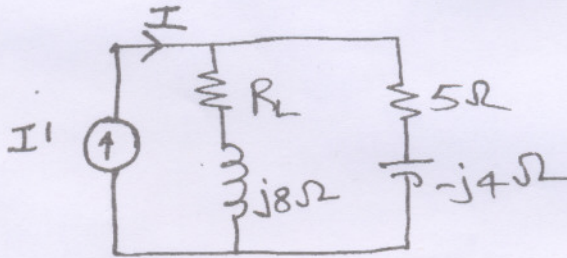b) Determine the value of R_L for resonance in the network shown. Also calculate the dynamic resistance. 5



17. a) A balanced 3ϕ load is connected to a balanced 3ϕ voltages of $230\ \text{volts}$ between lines and is instrumented for power measurement using two wattmeter method. The phase sequence is ABC. The wattmeter in line A reads $2.5\ \text{KW}$ and in line B reads $0.5\ \text{KW}$. Calculate the

- Power factor of the load
- Line current and
- Load impedances assuming star connection. 5

b) Three identical impedances of $18\ \angle_{-30^\circ}\ \Omega$ in delta and three impedances of $10\ \angle_{45^\circ}\ \Omega$ in star are both connected to same 3ϕ 3 wire, $440\ \text{V}$ system. Find the magnitude of line current and total power. 5