

FACULTY OF ENGINEERING

B.E. II/IV Year (E & EE) II Semester (Main) Examination, May/June 2011


ELECTRICAL CIRCUITS - II

Time : 3 Hours]

[Max. Marks : 75

Answer **all** questions from Part A.Answer any **five** questions from Part B.**Part A** – (Marks: 25)1. Find the range of values 'a' in $P(s)$. So that $P(s) = 2s^4 + s^3 + as^2 + s + 2$ is Hurwitz. 3

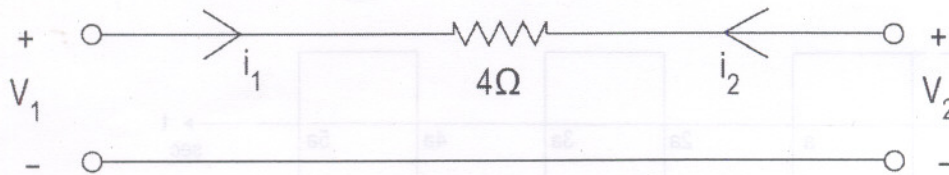2. Find the Y-parameters of the following network. 3



3. Define the term 'Symmetry'. 2

4. Define 'Band width' and its importance. 2

5. State and prove Final value theorem. 3

6. Express T - parameters in terms of h - parameters. 2

7. Define the term "Network Synthesis"? 2


8. Obtain the Laplace Transform of "t cos at". 3

9. List the properties of Positive-Real function. 2

10. Explain the effect of addition of zero at infinity in the transfer function and also explain how it effects the actual circuit. 3

Part B – (Marks: 50)11. Show that, when two 2-port networks N_1 and N_2 are connected in cascade the equivalent ABCD parameters of the combined network is the product of ABCD parameters of each, individual 2 port Network. 10

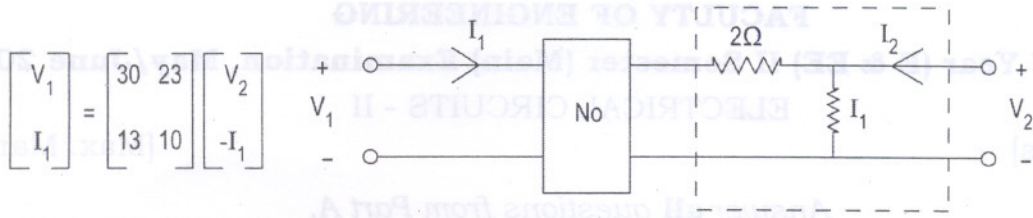12. In the arrangement of figure given below.



Find the transmission parameters of No?

10


13. The Fourier Transform of a continuous time signal $f(t)$ is given by

$$F(\omega) = \frac{10}{j\omega + 4}. \text{ Determine the Fourier transform } Y(\omega) \text{ if } Y(t) = f(t) \cos 2t.$$

10

14. (a) Find the Laplace transform of the following rectangular wave form.

6

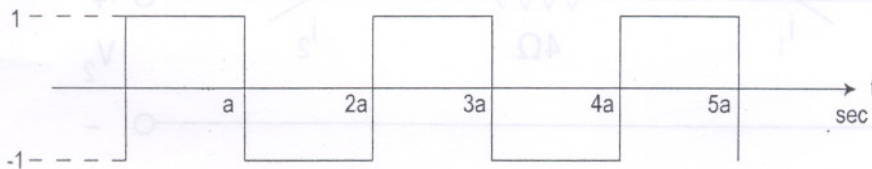

(b) Obtain the Laplace transform of $e^{-t}(1 + \cos 2t)$.

4

15. The driving point impedance of an LC network is given by $Z(s) =$

$$z(s) = \frac{10(s^r + 4)(s^r + 16)}{s(s^r + 9)}$$

Obtain the first form of Foster network.

10

16. Check whether the following functions is Hurwitz or not.

10

(a) $P(s) = s^4 + s^3 + 3s^2 + 2s + 2.$

(b) $Q(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4.$

17. Given the driving point impedance function

$$z(s) = \frac{s(s^r + 2)}{(s^r + 1)(s^r + 4)}$$

Synthesize a ladder network of the first cauer form and second cauer form for this impedance function.

10