

FACULTY OF ENGINEERING
B.E. 2/4 (EE/Inst.) (Semester – I) (New) (Main) Examination, January 2012
ELECTRONIC ENGINEERING – I

Time : 3 Hours]

[Max. Marks : 75


Note : Answer *all* questions from Part A, answer *any five* questions from Part B.

PART – A



(25 Marks)

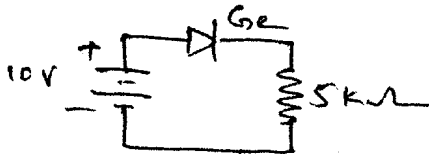1. Determine the current flowing in the circuit in figure 1.



2

2. What are the drawbacks of bridge rectifier over centre-tap rectifiers ? 3
3. A BJT has $I_B = 10 \mu\text{A}$, $\beta = 99$ and $I_{CO} = 1 \mu\text{A}$. What is its collector current I_C ? 3
4. Why CC transistor configuration is seldom used ? 2
5. In a JFET the drain current changes from 1.2 mA to 1.5 mA when the gate to source voltage is varied from -4.25 V to -4.10 V , keeping the drain-source voltage constant. Determine the transconductance for the given JFET. 3
6. Sketch the VI characteristics of a SCR. 2
7. What do you understand by the cascade configuration ? 3
8. Draw any one of the low frequency BJT amplifier circuit. 2
9. What is the effect of emitter (source) bypass capacitor on LF response with respect to multistage amplifiers ? 3
10. List out the salient features of multistage amplifiers. 2

PART – B

(50 Marks)

11. a) A single phase fullwave rectifier makes use of π -section filter with two $10\mu\text{F}$ capacitors and a choke of 10 H. The secondary voltage is $280 V_{\text{rms}}$ with respect to centre tap. If the load current is 100 mA, determine the dc output voltage and percentage ripple in the output. Assume supply frequency of 50 Hz. 7
- b) What is the purpose of bleeder resistance in a rectifier circuit using L-C filter ? 3
12. a) Explain the difference between ac and dc load line. Derive the load line equation of a BJT in CE configuration. 5
- b) Draw the circuit of a CE amplifier with emitter bias. Derive the relation for stability factor for such a circuit. 5
13. a) Describe the construction and operation of a MOSFET in depletion region. 5
- b) Prove that the transconductance g_m of a JFET is given by $g_m = \frac{2}{|V_p|} \sqrt{I_{DS} I_{DSS}}$, where V_p = pinch-off voltage, I_{DS} = drain current, $I_{DSS} = \text{max. } I_{DS}$ corresponding to $V_{GS} = 0$ volt. 5
14. Discuss in detail about Miller's theorem and difference amplifier. 10
15. Explain with neat diagrams about the frequency response of RC and transformer coupled amplifiers. 10
16. a) Compare DIAC and TRIAC. 5
- b) Explain about zener and avalanche breakdowns. 5
17. Write short note on the following :
- a) h-parameters 5
- b) UJT. 5