

FACULTY OF INFORMATICS
B.E. 2/4 (IT) I Sem. (New) (Main) Examination, Dec. 2011/Jan. 2012
MICRO ELECTRONICS

Time: 3 Hours]

[Max. Marks: 75

Note : Answer *all* questions from **Part A**. Answer *any five* questions from **Part B**.

PART - A

(25 Marks)



1. Briefly explain the operation of Schottky diode. 3
2. List the applications of cathode ray oscilloscope. 2
3. Compare the doping levels of emitter, base and collector. 2
4. What is pinchoff voltage ? What is its significance ? 3
5. Derive the expression for voltage gain in negative feedback. 3
6. Define Barkhausen criteria. 2
7. List the ideal characteristics of op-amp. 3
8. Draw the circuit for integrator using op-amp. 2
9. What is noise margin ? 2
10. Briefly explain about CMOS logic. 3

PART - B

(50 Marks)

11. a) Explain about clipping and clamping circuits. 6
b) Explain about conduction in semi-conductors. 4
12. a) Explain about the physical structure and modes of operation of BJT. 6
b) Explain about different regions of operation of MOSFET. 4
13. a) Discuss the properties of negative feedback. 6
b) Explain the operation of Hartley oscillator. 4



- 14. a) Write about the operation of square wave generator. 6
 - b) How an op-amp can be used as logarithmic amplifier ? 4
 - 15. a) Explain the CMOS implementation of 2-input NOR gate and exclusive OR gates. 4
 - b) Discuss about the basic structure of PUN and PDN. 6
 - 16. a) Explain how a zener diode can be operated as voltage regulator. 5
 - b) Draw the small signal equivalent models of BJT. 5
 - 17. Write short notes on :
 - a) RC oscillator. 3
 - b) CCVS using op-amp. 4
 - c) VTC of inverter. 3
-